

الجامعة الألمانية الأردنية
German Jordanian University

Power Electronics Pre-Lab

Controlled Single Phase Rectifiers

By:

Ramez Al-Masadeh

Instructor:

Eng-Anas Alswaeer

Single Phase Controlled Full-Wave Rectifier

Circuit: 3-Phase Half-Wave Uncontrolled Rectifier

Parameter	Symbol	Value
Source Phase Voltage (RMS)	*V_s*	90 V
Source Frequency	*f*	50 Hz
Load Resistance	*R*	100 Ω
Average Output Voltage	*Vdc*	49.5 V
Average Output Current	*Idc*	0.4928 A

Circuit Diagram

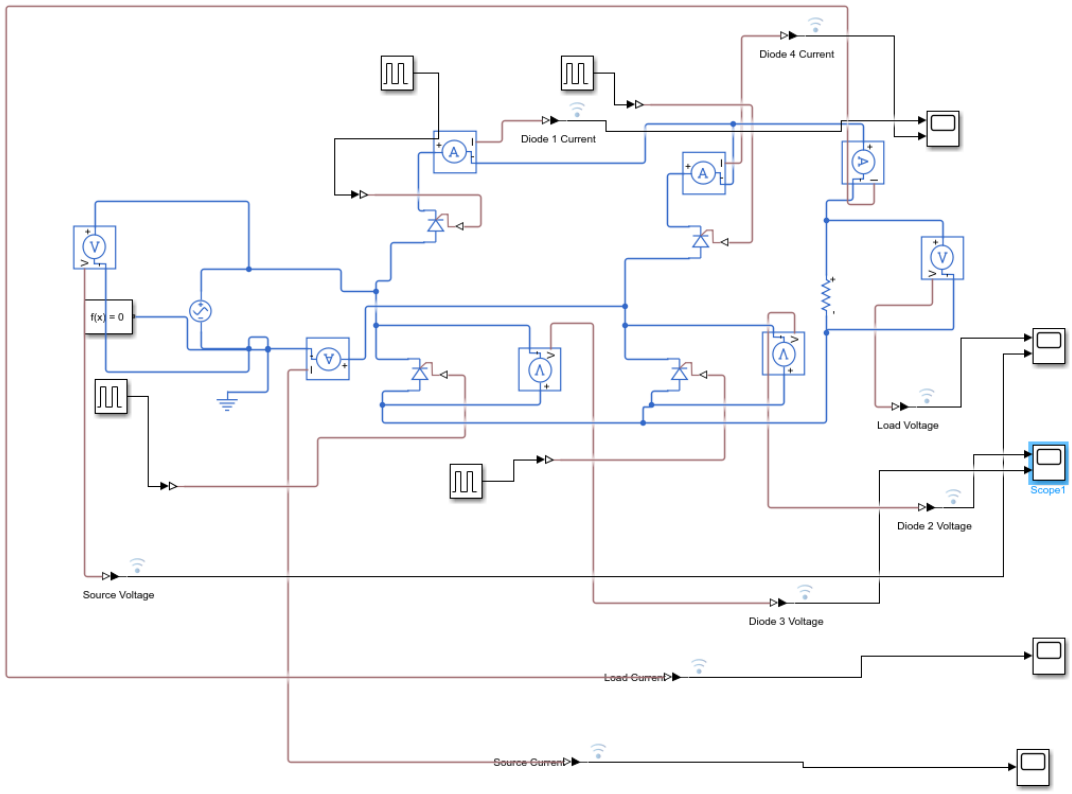


Figure 1 Single Phase Controlled Full-Wave Rectifier

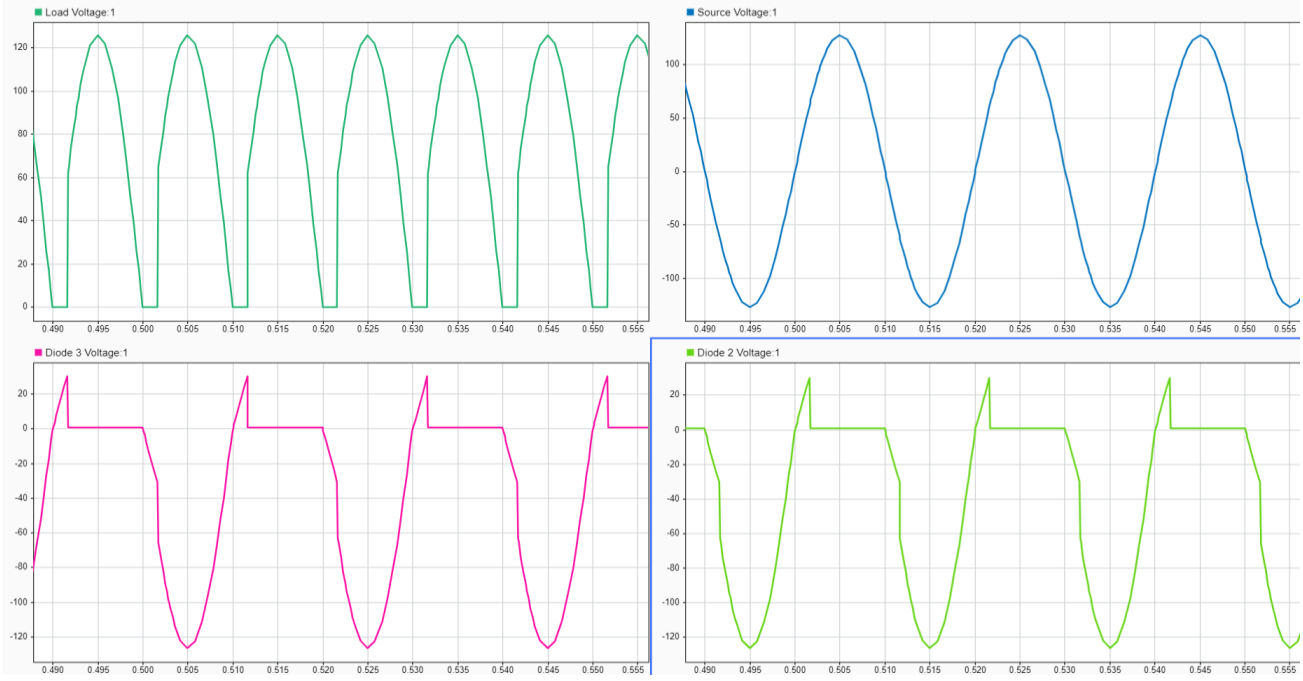


Figure 2 —Voltage Wave forms

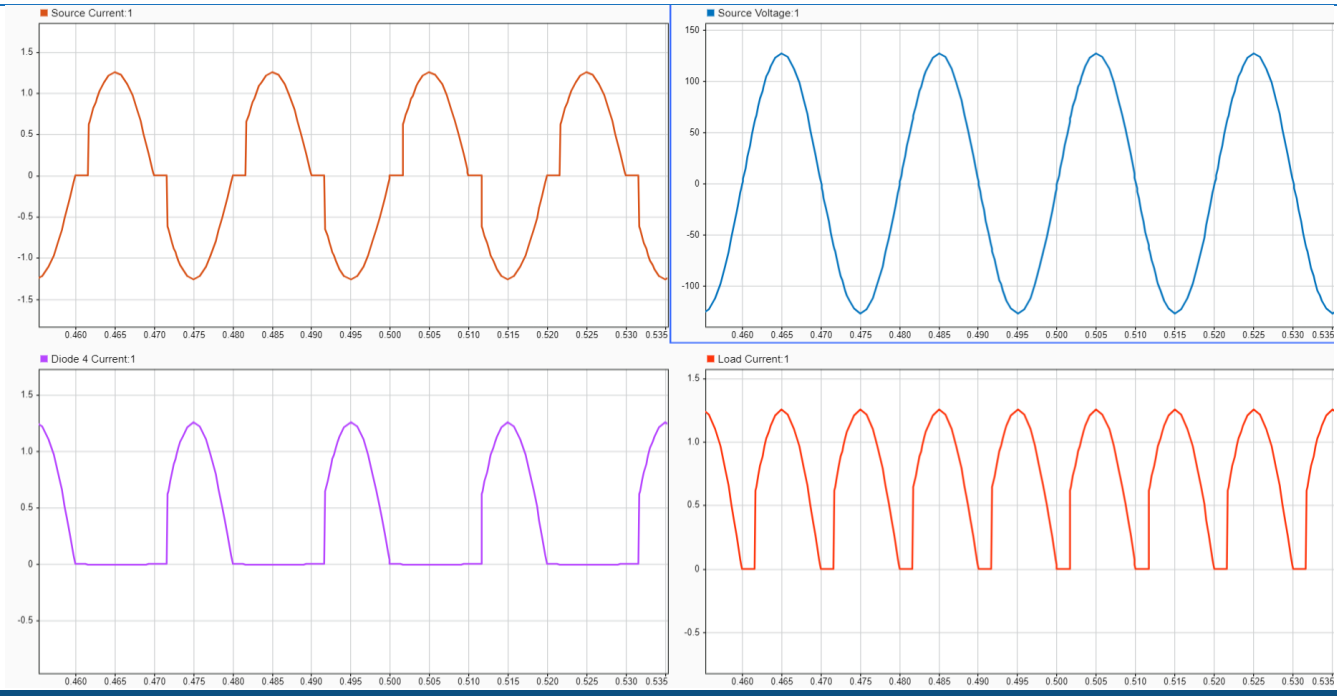


Figure 3 —Current Wave forms